

impedance is around 5 k . Sinking too much of current from

Although differential input rejects commonmode noise inherently, the commonmode voltage on each of the input pin still affects the operation of the controller. A commonmode filter is generally implemented to filter out the commonmode noise. Figure 11. shows a schematic of the commonmode filter. Bandwidth of the commonmode filter is

$$f_{BW-comon} = \frac{1}{2 \cdot R_f \cdot C_c} \quad (\text{eq. 7})$$

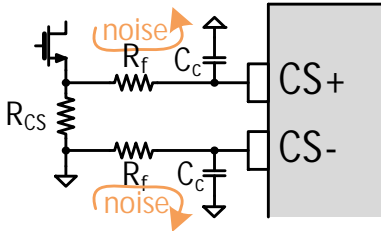


Figure 11. Common mode Filter for CS Pin

Due to a mismatch between the resistors and capacitors in the commonmode filter, commonmode noise may be filtered differently between CS+ and CS-. As a result, a differentialmode noise appears on the CS signals. To tackle with the differentialmode noise, we add a capacitor to filter out the differentialmode noise.

With the resultant CS filter in Figure 12, which combines commonmode and differentialmode filters, the bandwidth of a lowpass filter for the differential CS signals becomes

$$f_{BW-diff} = \frac{1}{2 \cdot 2R_f \cdot C_d + \frac{1}{2} \cdot C_c} \quad (\text{eq. 8})$$

The bandwidth of the filter should be set based on noise that is generated in actual design results. In a 5 kW reference design for FAN9673 with 40 kHz of switching frequency, we set $f_{BW-diff}$ at 154 kHz and $f_{BW-comon}$ at 51.3 kHz.

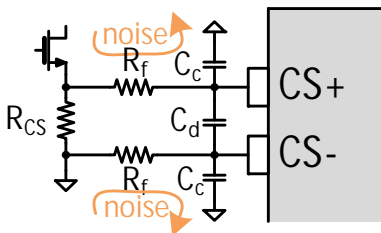


Figure 12. CS Pin Filter

Effect of Input Range Setting

VIR pin of FAN967x sets two different modes that optimize for universal input range and European input range, respectively. This pin sources a constant current.

A resistance value connecting between VIR and GND decides the voltage on the VIR pin. The voltage on the VIR pin needs to be set higher than 3.5 V or lower than 1.5 V. Avoid anything in between.

The setting on the VIR pin changes some internal signals of FAN967x, which are collected in Table 1. A constant appears in the table. According to the test cases of VLPK, which can be found in electrical characteristics in the datasheet, KLPK is 2.465.

Table 1. Effects of VIR Setting

V _{VIR}	< 1.5 V	> 3.5 V
Optimized for	Universal input range (90~264 Vac)	European input

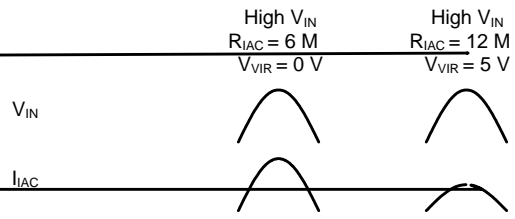


Figure 16. V_{IN} Related Signals under Different V_{IR} and R_{IAC} Setting

To make inductor track current command well, the bandwidth of the current tracking loop need to set high enough. When the complex pole formed by L and C_{OUT} is at a frequency much lower than the control bandwidth of $T_i(s)$

AND9925/D

$$\text{Loopgain}(s) = \frac{(V_{IN.PEAK} |\sin(\omega t)|)^2}{V_{IN.RMS}^2} \frac{1}{V_{OUT}} \frac{1}{s} \frac{1}{C_{OUT}} \frac{P_{MAX}}{(V_{VEA.MAX} \cdot 0.6)} \frac{V_{FBPFC}}{V_{OUT}} G_{mv}(s) \quad (\text{eq. 25})$$

$$\text{Loopgain}(s)_{ac \text{ cycle}} = \frac{1}{s} \frac{1}{C_{OUT}} \frac{P_{MAX} I_{OUT}}{(V_{VEA.MAX} \cdot 0.6) V_{OUT}}$$

